

# Finite State Machines

**CS 64: Computer Organization and Design Logic**  
**Lecture #16**


Ziad Matni  
Dept. of Computer Science, UCSB

# Lecture Outline


---

- Review of Latches vs. FFs
- Finite State Machines
  - Moore vs. Mealy types
  - State Diagrams
  - “One Hot” Method

# Latches vs. FFs

 

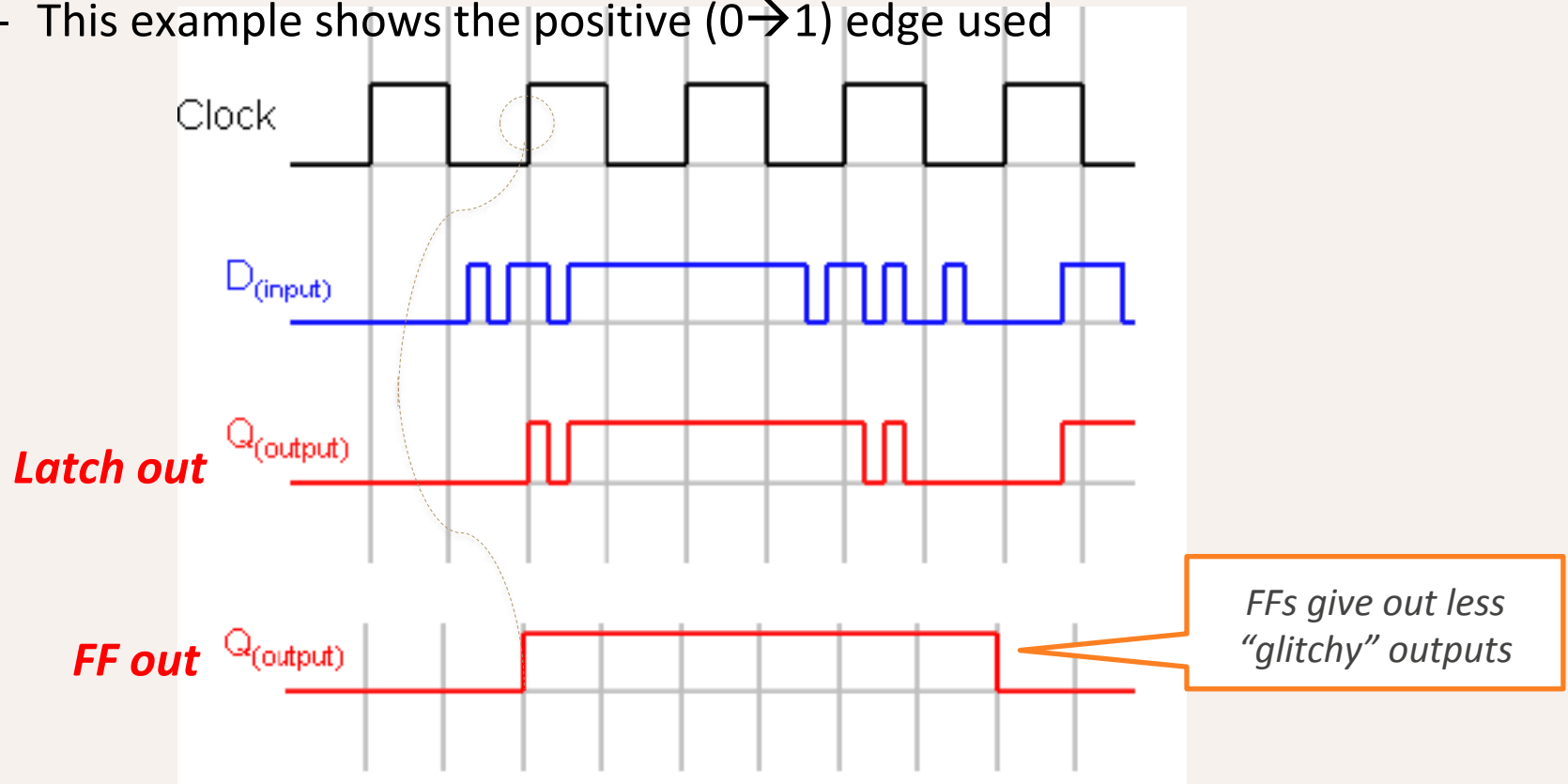- Latches capture data on an **entire 1 or 0 level of the clock**
- FFs capture data on the **edge of the clock**
  - This example shows the positive (0→1) edge used




If a combinational logic circuit is an implementation of a ***Boolean function***,

then a sequential logic circuit can be considered an implementation of a ***finite state machine***.

# Finite State Machines (FSM)

- An **abstract machine** that can be in **exactly one of a finite number of states at any given time**
  - It's a very simple model of a computational machine, unlike Pushdown Automata and Turing Machines
    - You'll discover these in other CS upper-div classes
- The FSM can change from one state to another in **response to some external inputs**
- The change from one state to another is called a **transition**.
- An FSM is defined by a list of its states, its initial state, and the conditions for each transition.


# Example of a Simple FSM: The Turnstile

 

## State Transition Table

Current State	Input	Next State	Output
Locked	Coin	Unlocked	Unlocks the turnstile so that the customer can push through.


# Example of a Simple FSM: The Turnstile

 

## State Transition Table


Current State	Input	Next State	Output
Locked	Coin	Unlocked	Unlocks the turnstile so that the customer can push through.
Locked	Push	Locked	Nothing – you're locked! 😊
Unlocked	Coin	Unlocked	Nothing – you just wasted a coin! 😊
Unlocked	Push	Locked	When the customer has pushed through, locks the turnstile.

# General Form of FSMs

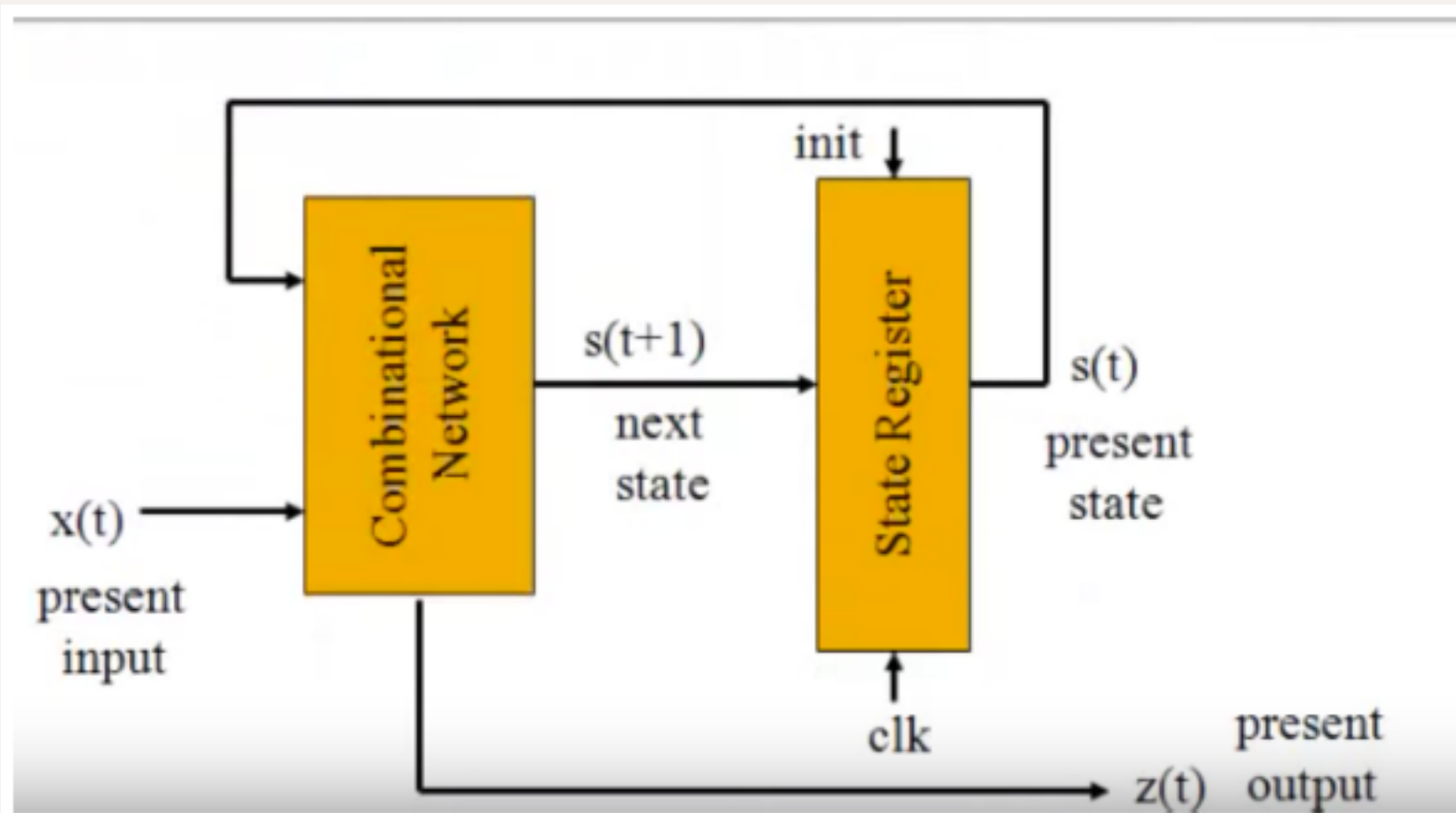



# Example

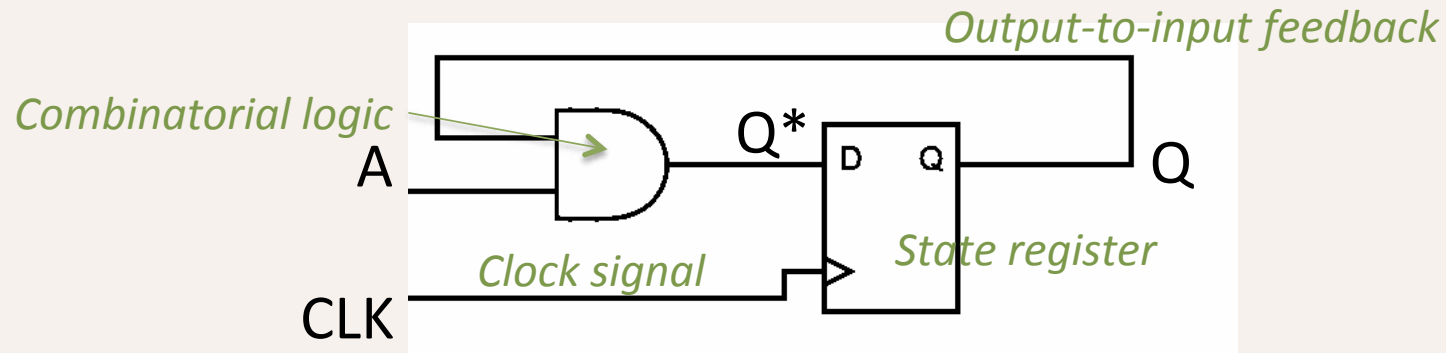

$$Q^* = Q_0 \cdot A$$


On the next rising edge of the clock, the output of the D-FF  $Q$  ( $Q^*$ ) will become the previous value of  $Q$  ( $Q_0$ ) **AND** the value of input  $A$

# FSM Types


**There are 2 types/models of FSMs:**

- **Moore machine**
  - Output is function of present state only
- **Mealy machine**
  - Output is function of present state *and* present input

# Moore Machine

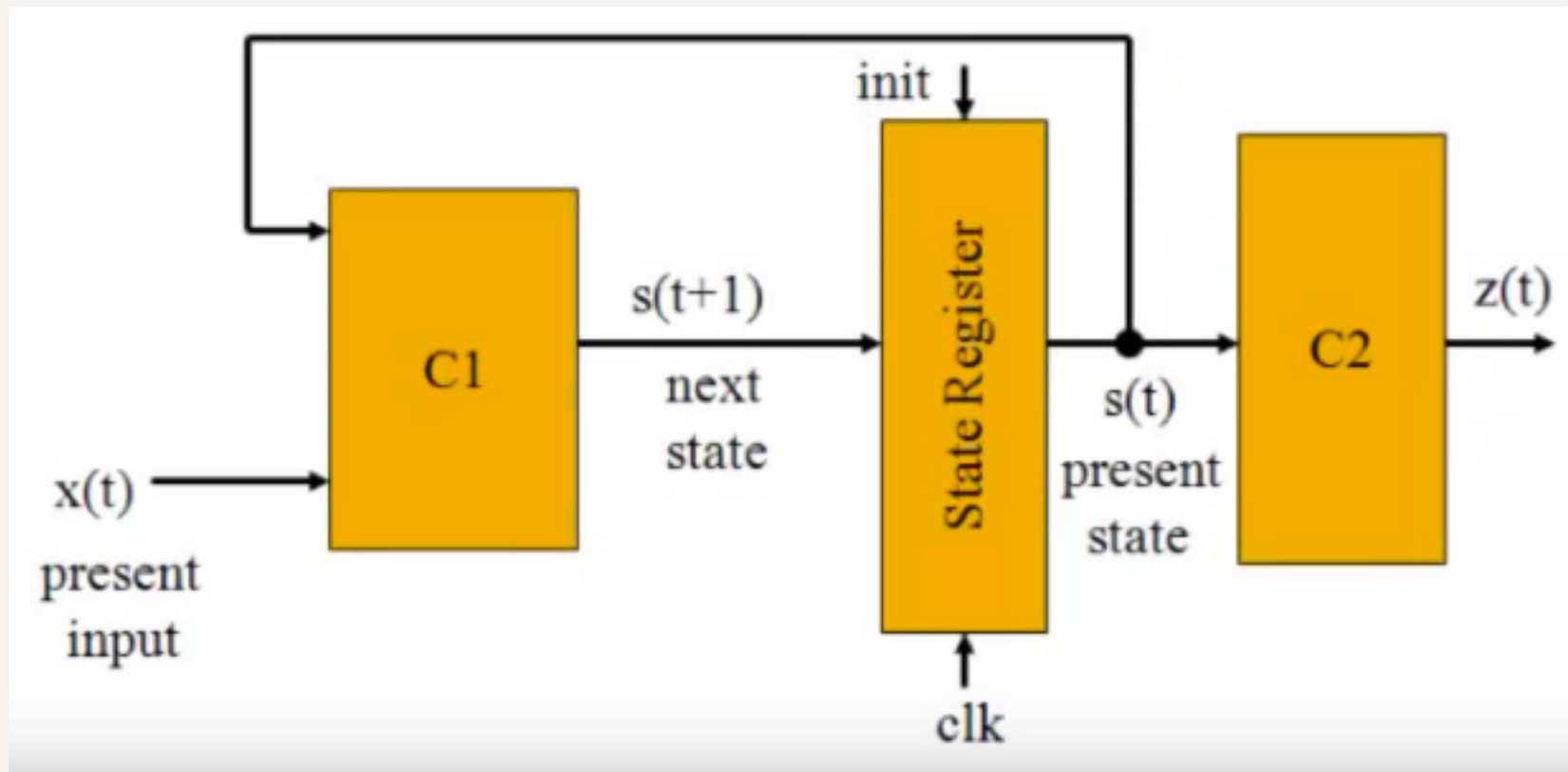

 
# Example of a Moore Machine (with 1 state)




$$Z = \overline{(Q^* + B)} = \overline{(Q_0 \cdot A + B)}$$

On the next rising edge of the clock, the output of the entire circuit (Z) will become  
(the previous value of Q ( $Q_0$ ) **AND** the value of input A)  
**NOR B**

# Mealy Machine

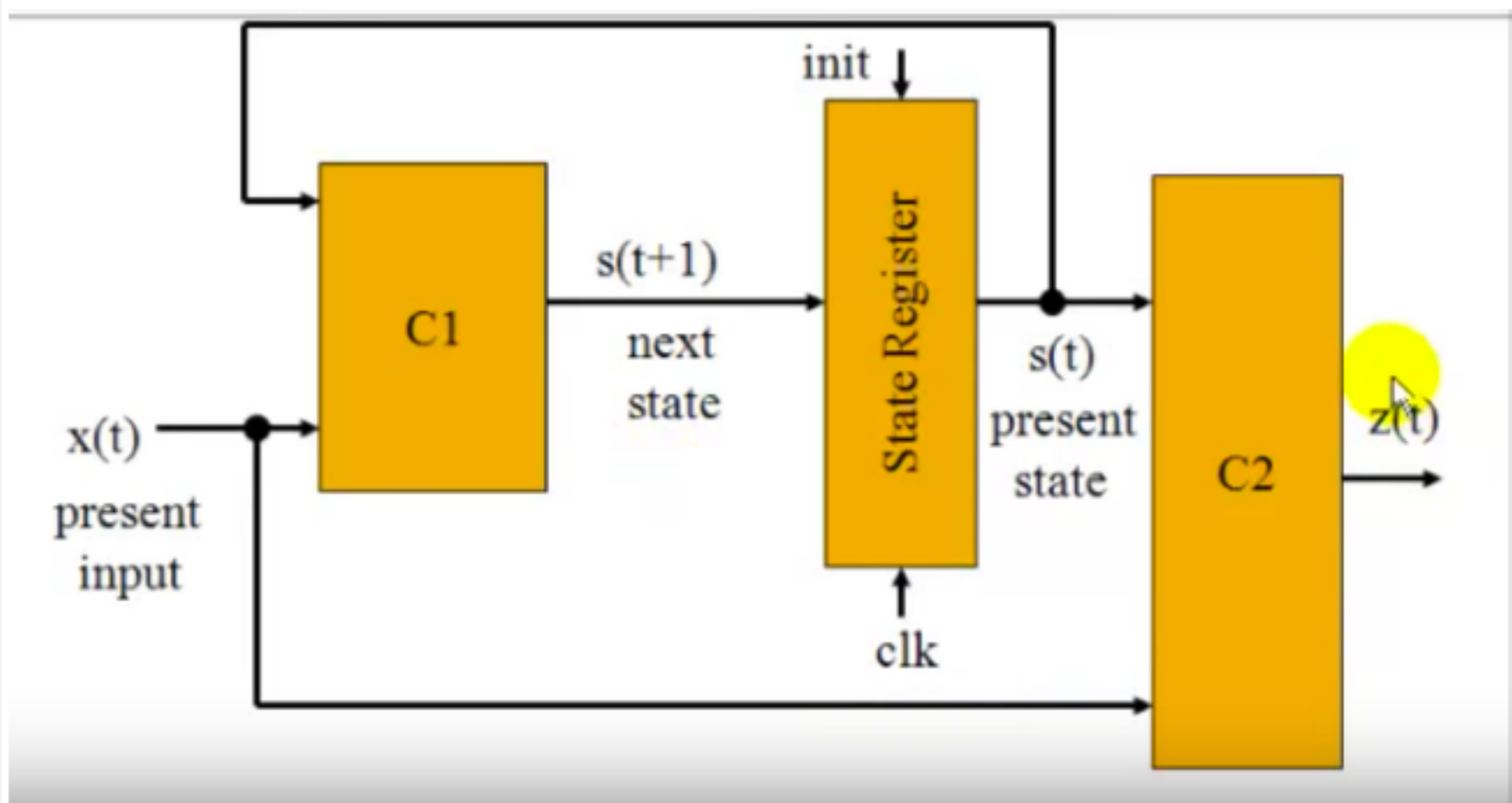
 
# Example of a Mealy Machine (with 1 state)




$$Z = (Q^* + A + B) = (Q_0 \text{ XOR } A) + (A + B)$$

On the next rising edge of the clock, the output of the entire circuit (Z) will become ...etc...
 
# Diagramming State Machines

- A simple FSM example
- 2 states:
  - Door opened
  - Door closed
- This is called a **state diagram**



# Example of a Moore Machine 1

## WASHER\_DRYER

- Let's "build" a sequential logic FSM that acts as a controller to a washer/dryer machine

SO:

- Before we begin, the machine is in an initial state that is waiting for you to insert a coin. We'll call that state the "Initial State" (inventive, no?)
- The machine will start a washer timer as soon as a coin is inserted. The timer is controlled by a signal (i.e. input var) called **TIMER\_LT\_30**, which is always initialized to be 1.



# Example of a Moore Machine 1

## WASHER\_DRYER

- Upon inserting a coin in the machine, we will begin the *wash cycle*. We'll call that state "Wash".
- This state will output a signal to fill the washer with water (**FILL\_WATER**).
- As long as the timer is below 30 mins (**TIMER\_LT\_30 = 1**), the cycle continues.
- When the timer surpasses 30 mins (i.e. **TIMER\_LT\_30 = 0**), this state will end

# Example of a Moore Machine 1

## WASHER\_DRYER


- When the timer hits 30 mins, we will begin the *rinse cycle*. We'll call that "Rinse".
- This will output a signal to drain the water and refill with new water (**DRAIN\_REFILL = 1**).
- As long as the soap sensor is on (**SOAP = 1**), the cycle continues.
- When the soap sensor turns off (i.e. **SOAP = 0**), this state will end

# Example of a Moore Machine 1

## WASHER\_DRYER

- When the soap sensor goes off, we will begin the *dry cycle*. We'll call that "Dry".
- This state will output a signal to drain the water and begin drying (**DRAIN = 1**).
- As long as the wet clothes sensor is on (**WET = 1**), the cycle continues.
- When the wet clothes sensor is off (**WET = 0**), we will stop!
- This means going back to the "Initial State"

# State Diagram 1

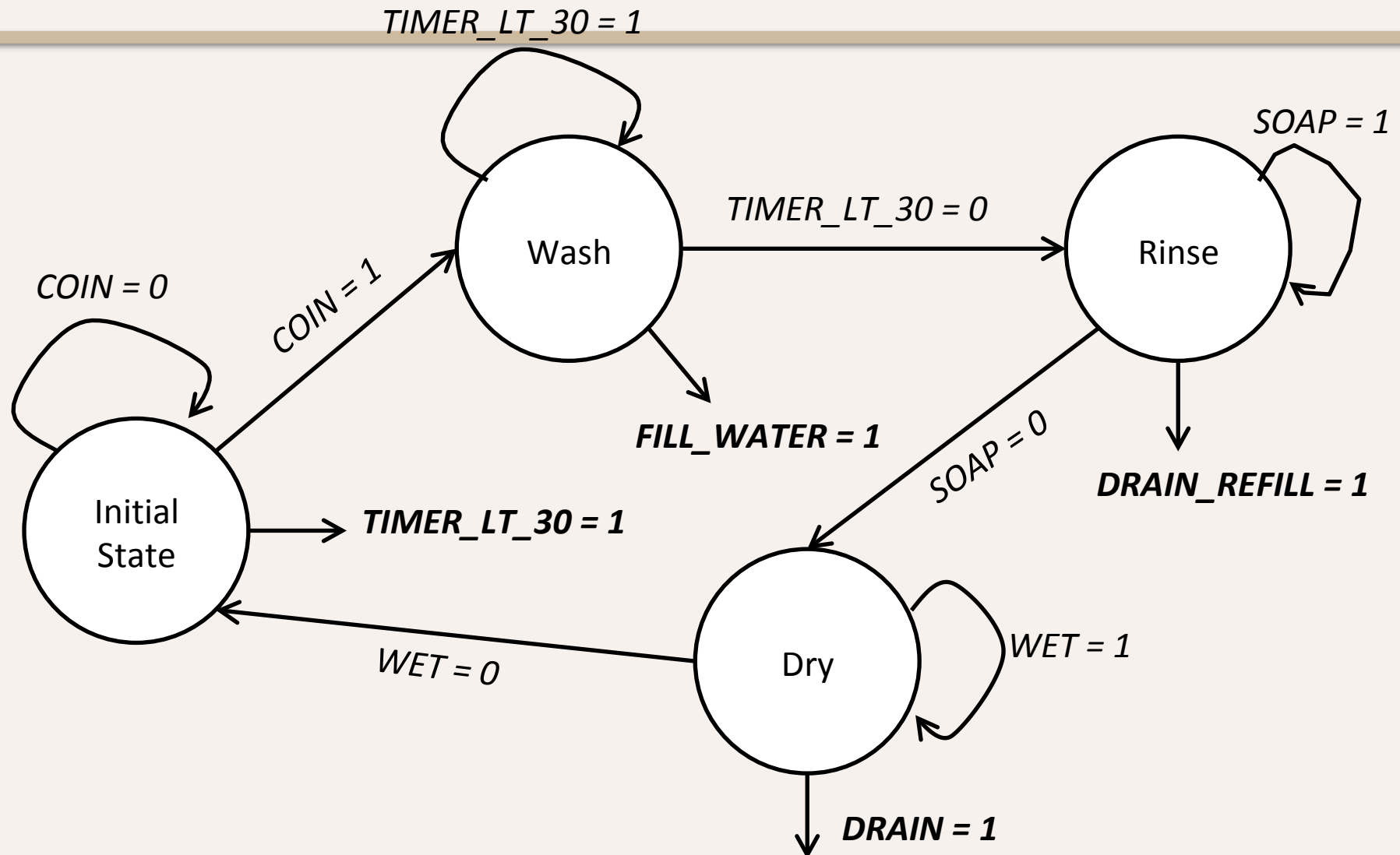

# Example of a Moore Machine 2


## DETECT\_1101

- Let's build a sequential logic FSM that always detects a specific serial sequence of bits: **1101**

S0:

- We'll start at an "Initial" state (S0)
- We'll first look for a **1**. We'll call that "State 1" (S1)
  - Don't go to S1 if all we find is a **0**!
- We'll then keep looking for another **1**. We'll call that "State 11" (S2)
- Then... a **0**. We'll call that "State 110" (S3)
- Then another **1**.  
We'll call that "State 1101" (S4) – this will output a **FOUND** signal
- We will always be detecting "1101" (it doesn't end)

# State Diagram 2

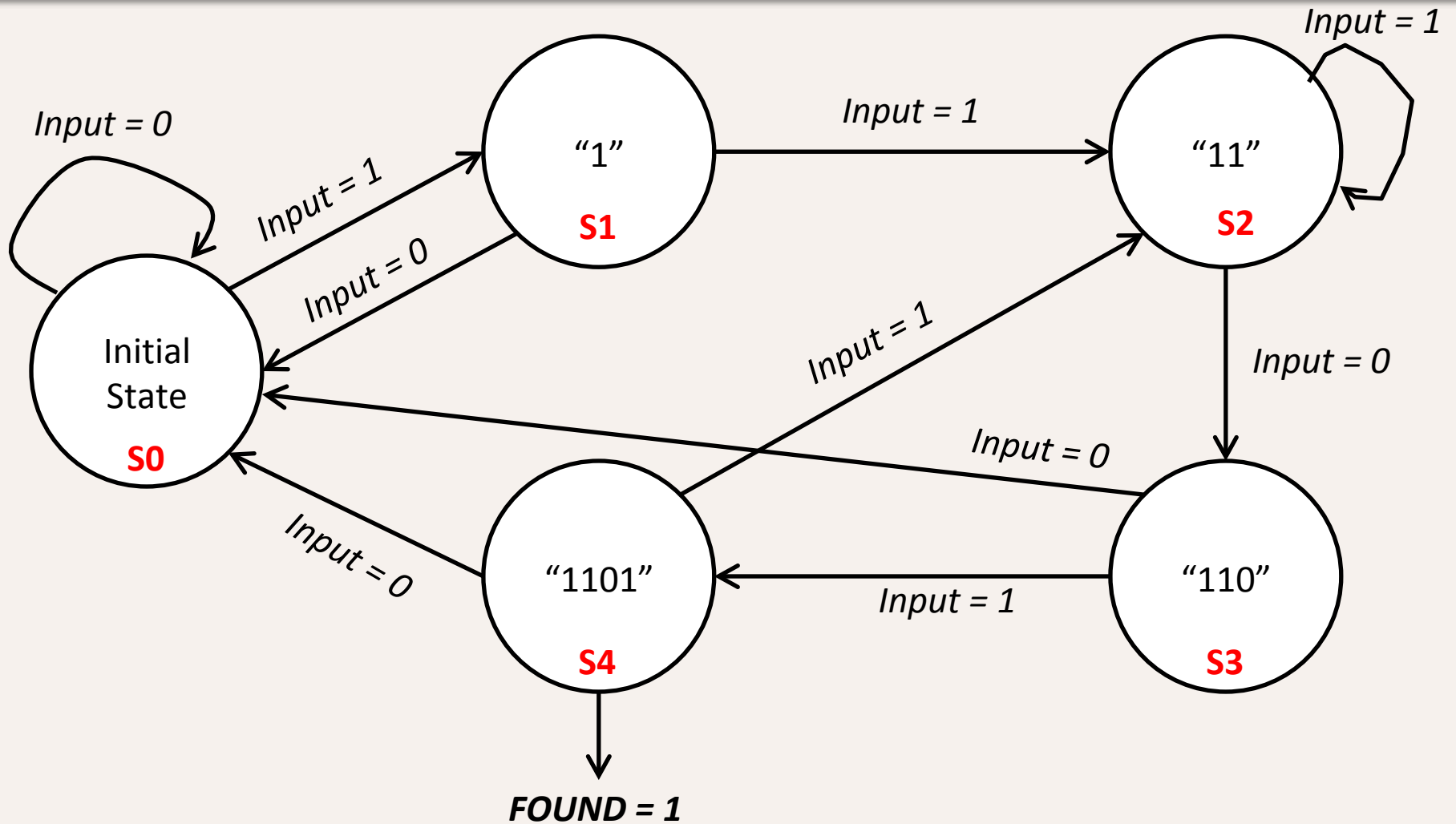

# Going from State Diagram to Circuit

- There's more than 1 way to do this, but the most popular is the “**One Hot Method**”
- Give each state it's own D-FF output
  - # of FFs needed = # of states
- Inputs to the FFs are combinatorial logic that can be simplified into a “sum-of-products” type of Boolean expression
- Current CAD software can do this automatically
- Implementation is usually done on a simulator (software), or prototype hardware Integrated Circuit (FPGA)

# Encoding our States

*Per the last example:* We had 5 separate states:

NAME		Binary Code	<u>"One Hot" Code</u>	OUTPUT
• Initial State	S0	000	00001	
• "1"	S1	001	00010	
• "11"	S2	010	00100	
• "110"	S3	011	01000	
• "1101"	S4	100	10000	FOUND

- Advantage of this "One Hot" approach?
  - When we implement the machine with circuits, we can use a D-FF for every state (so, in this example, we'd use 5 of them)



# Using the “One Hot” Code to Determine the Circuit Design

- Every state has 1 D-FF
- We can see that (follow the arrows!!):


$$S1^* = S0.I$$

$$S2^* = S1.I + S2.I + S4.I$$

$$S3^* = S2.\bar{I}$$


$$S4^* = S3.I$$
 
$$S0^* = S0.I + S1.\bar{I} + S3.\bar{I} + S4.\bar{I}$$



also, when S4 happens, FOUND = 1, i.e. **FOUND = S4**

# Implementing the Circuit

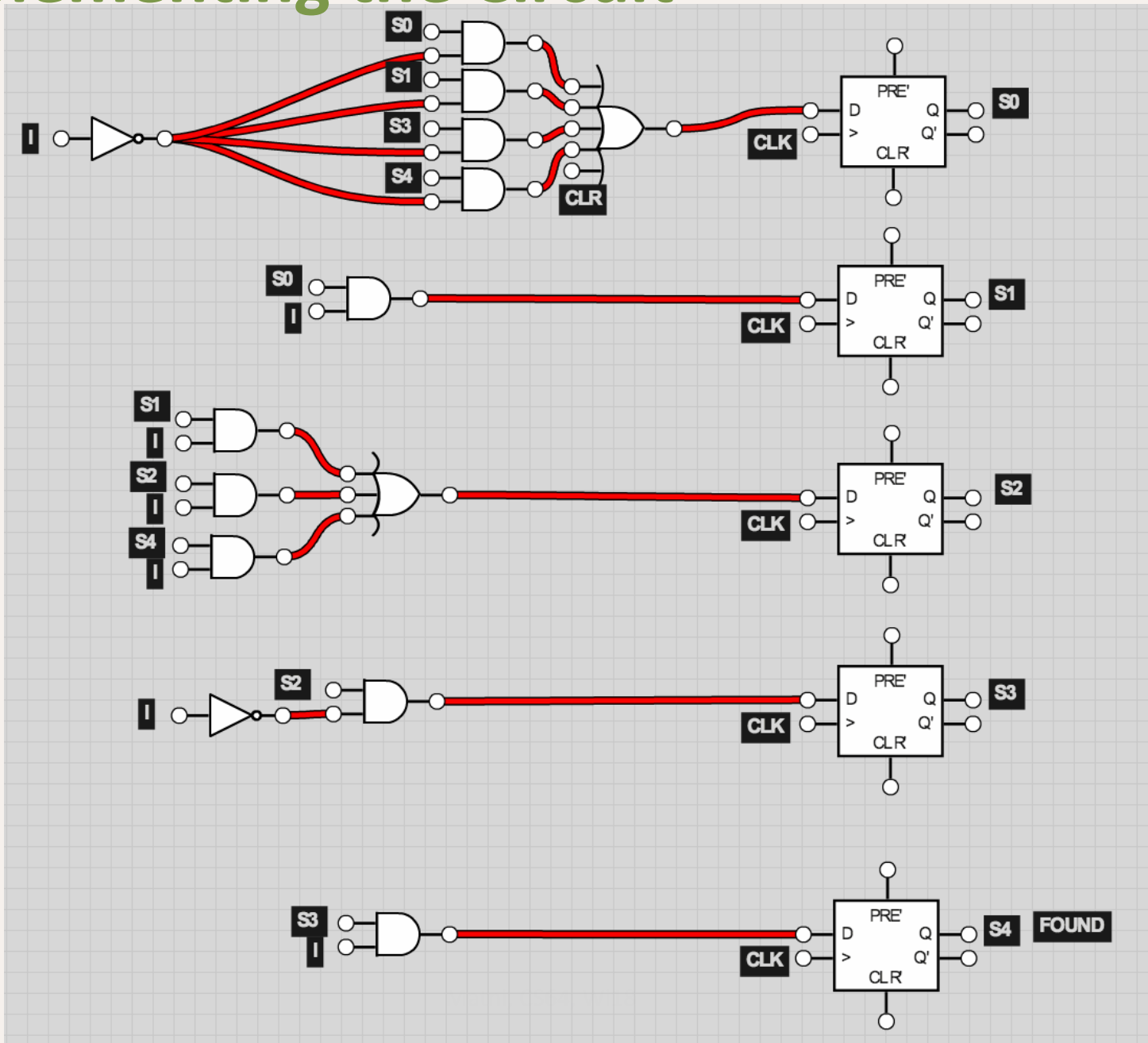

# Your To Dos

---

- Lab #8 is due end of day Friday

**</LECTURE>**